 


KARTHICK RAJA B
126004121

Given:

This is a Moore state machine with two states, two inputs, and one output. Implement this state machine.



Verilog Code:

```
module moore_machine (
    input clk,
    input reset,
    input j,
    input k,
    output reg out
);
    parameter OFF = 1'b0;
    parameter ON = 1'b1;

    reg current_state, next_state;

    always @(posedge clk or posedge reset) begin
        if (reset)
            current_state <= OFF;
        else
            current_state <= next_state;
    end

    always @(*) begin
```

```

case (current_state)
  OFF: begin
    if (j)
      next_state = ON;
    else
      next_state = OFF;
  end

  ON: begin
    if (k)
      next_state = OFF;
    else
      next_state = ON;
  end

  default: next_state = OFF;
endcase
end

```

```

always @(*) begin
  case (current_state)
    OFF: out = 0;
    ON: out = 1;
    default: out = 0;
  endcase
end

```

endmodule

Testbench code:

```

`timescale 1ns / 1ps
module moore_machine_tb();
  reg clk;
  reg reset;

```

```

reg j;
reg k;
wire out;
moore_machine uut (
    .clk(clk),
    .reset(reset),
    .j(j),
    .k(k),
    .out(out)
);
always #5 clk = ~clk;
initial begin
    clk = 0;
    reset = 1;
    j = 0;
    k = 0;
    #10;
    reset = 0;
    #10 j = 1;
    #10 j = 0;
    #10 k = 1;
    #10 k = 0;
    #10 j = 1;
    #10 j = 0;
    #10 reset = 1;
    #10 reset = 0;
    #10;

    $finish;
end

endmodule

```

Functional Simulation:

